

Manufactured by TELEFUNKEN (Germany) テレフンケン社 IC 商品


TELEFUNKEN electronic
 Creative Technologies

MANUFACTURED BY TELEFUNKEN (GERMANY)

東光株式会社、テレフンケン社(ドイツ)の代理店です。

Part No.	Contents		
TV & VTR	U2200B-FP	VHF mixer and UHF IF post amplifier	
	U2300B-FP	VHF/UHF TV tuner	
	U4744B	SAW filter driver	
	U4477B	VHF mixer and UHF IF post amplifier	
	TDA4426	Video IF amplifier with AFC	
	TDA4439	Multistandard video IF amplifier with AFC	
	TDA4452	Multistandard video IF amplifier with VTR plug (DIN), ESD Protected	
	TDA4453BG	Video IF amplifier for multistandard TV sets and VTR applications, high video bandwidth	
	TBA120S	FM IF amplifier and detector	
	TBA120T	FM IF amplifier and detector for ceramic resonator	
	TBA120U	FM IF amplifier and detector for coils	
	TDA4445A	Quasi parallel sound processor with quadrature demodulator	
	TDA4480-D	Multistandard quasi parallel sound processor, ESD Protected	
	TDA4481-C	Multistandard quasi parallel sound processor for mono TV sets, SCART switch and volume control, ESD Protected	
	TDA4482-C	Quasi parallel sound processor for TV stereo application, ESD Protected	
	U829BS	FM IF amplifier and demodulator for TV stereo sound processing	
	U2829B	Double FM IF amplifier and demodulator for TV stereo sound processing, ESD Protected	
	U2840B	FM IF amplifier and demodulator with SCART	
	U4490B	Sound IF circuit and mixer for SAT-TV, ESD Protected	
	TDA3505G	Analog controlled video processors	
	TDA4555/56	Multistandard decoder for PAL, SECAM, NTSC, ESD Protected	
	U4648B	I ² C bus controlled video processors for color TV receivers, ESD Protected	
	U8060B	PAL decoder	
	U8442B	Quad 6 bit D/A converter with I ² C bus	
	Power Control	TEA1007	Open loop power control for universal and condenser motors
		U208B	Open loop phase control of a.c. loads
U210B		Speed setting with load current compensation of tachless universal motors	
U211B		Feedback speed and torque control for universal and other a.c. motors	
U2008B		Low cost speed regulator, Load inrush current limitation for large motors, etc.	
U2010B		Universal motor control with load current compensation	
UAA145/146		Phase control in three phase network	
U490B		One shot power control for electric stapler devices	
Telecommunication		U448B	Amplifier for piezoelectric microphones
	U4056B	Electronic speech circuit for telephone sets, modem and telephone responder	
	U4058B	Low voltage speech circuit with line powered loudspeaker amplifier	
	U4071B	Two tone ringer for telephone sets, signal generator in cars and toys	
	U4072B	Two tone ringer for telephone sets, signal generator in cars and toys	
	U4074B	Tone ringer interface	
	U4076B	Three tone ringer for telephone sets, signal generator in cars and toys	
	U4077B	Three tone ringer for telephone sets, signal generator in cars and toys	
	U225B	Voltage limiter on symmetrical two wire speech branches in PABX	
	U2147B	Broadband compander circuits for noise reduction in radio telephones	
	U2790B	900MHz quadrature modulator for digital cellular radio systems	
	U2796B	900MHz mixer for cordless telephones	
	Automotive	U243B	Warning or car direction indicator, Lamp load $\geq 10W$
		U641B	Auto wiper control with two modes of operation, intermittent or wipe/wash operation
U6048B		Long term timer for radiator fan control	
U5000M		ABUS	
U6080B		Dashboard illumination dimmer	
U2227B	Driver circuit for ignition transmitter		